


# TTK 4155

## Industrial and embedded computer systems design

### Lecture #3

- Some basic topics in circuit design (continued...)
- Power supplies & voltage regulators
  - Shunt regulators
  - Linear regulators
  - Switching regulators
    - Inductor-based
    - Capacitor-based (charge pumps)
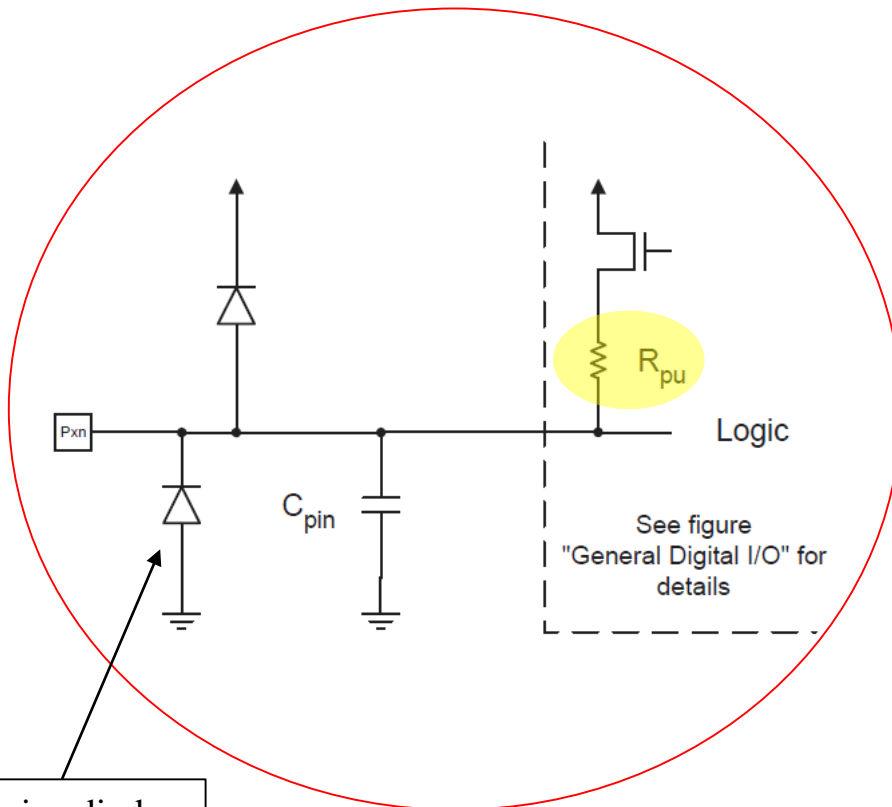
# Pull-up resistors on AVR ATmega microcontroller input ports



Clipping diodes  
(protection)

PDIP			
(OC0/T0) PB0	1	40	VCC
(OC2/T1) PB1	2	39	PA0 (AD0/PCINT0)
(RXD1/AIN0) PB2	3	38	PA1 (AD1/PCINT1)
(TXD1/AIN1) PB3	4	37	PA2 (AD2/PCINT2)
(SS/OC3B) PB4	5	36	PA3 (AD3/PCINT3)
(MOSI) PB5	6	35	PA4 (AD4/PCINT4)
(MISO) PB6	7	34	PA5 (AD5/PCINT5)
(SCK) PB7	8	33	PA6 (AD6/PCINT6)
RESET	9	32	PA7 (AD7/PCINT7)
(RXD0) PD0	10	31	PE0 (ICP1/INT2)
(TXD0) PD1	11	30	PE1 (ALE)
(INT0/XCK1) PD2	12	29	PE2 (OC1B)
(INT1/ICP3) PD3	13	28	PC7 (A15/TDI/PCINT15)
(TOSC1/XCK0/OC3A) PD4	14	27	PC6 (A14/TDO/PCINT14)
(OC1A/TOSC2) PD5	15	26	PC5 (A13/TMS/PCINT13)
(WR) PD6	16	25	PC4 (A12/TCK/PCINT12)
(RD) PD7	17	24	PC3 (A11/PCINT11)
XTAL2	18	23	PC2 (A10/PCINT10)
XTAL1	19	22	PC1 (A9/PCINT9)
GND	20	21	PC0 (A8/PCINT8)


## DC Characteristics

$T_A = -40^{\circ}\text{C}$  to  $85^{\circ}\text{C}$ ,  $V_{CC} = 1.8\text{V}$  to  $5.5\text{V}$  (unless otherwise noted)




Symbol	Parameter	Condition	Min.	Typ.	Max.	Units
$V_{IL}$	Input Low Voltage, Except XTAL1 and RESET pin	$V_{CC} = 1.8 - 2.4\text{V}$ $V_{CC} = 2.4 - 5.5\text{V}$	-0.5 -0.5		$0.2 V_{CC}^{(1)}$ $0.3 V_{CC}^{(1)}$	V
$V_{IH}$	Input High Voltage, Except XTAL1 and RESET pin	$V_{CC} = 1.8 - 2.4\text{V}$ $V_{CC} = 2.4 - 5.5\text{V}$	$0.7 V_{CC}^{(2)}$ $0.6 V_{CC}^{(2)}$		$V_{CC} + 0.5$ $V_{CC} + 0.5$	V
$V_{IL1}$	Input Low Voltage, XTAL1 pin	$V_{CC} = 1.8 - 5.5\text{V}$	-0.5		$0.1 V_{CC}^{(1)}$	V
$V_{IH1}$	Input High Voltage, XTAL1 pin	$V_{CC} = 1.8 - 2.4\text{V}$ $V_{CC} = 2.4 - 5.5\text{V}$	$0.8 V_{CC}^{(2)}$ $0.7 V_{CC}^{(2)}$		$V_{CC} + 0.5$ $V_{CC} + 0.5$	V
$V_{IL2}$	Input Low Voltage, RESET pin	$V_{CC} = 1.8 - 5.5\text{V}$	-0.5		$0.2 V_{CC}$	V
$V_{IH2}$	Input High Voltage, RESET pin	$V_{CC} = 1.8 - 5.5\text{V}$	$0.9 V_{CC}^{(2)}$		$V_{CC} + 0.5$	V
$V_{OL}$	Output Low Voltage <sup>(3)</sup> , Ports A, B, C, D, and E	$I_{OL} = 20\text{ mA}$ , $V_{CC} = 5\text{V}$ $I_{OL} = 10\text{ mA}$ , $V_{CC} = 3\text{V}$			0.7 0.5	V V
$V_{OH}$	Output High Voltage <sup>(4)</sup> , Ports A, B, C, D, and E	$I_{OL} = -20\text{ mA}$ , $V_{CC} = 5\text{V}$ $I_{OL} = -10\text{ mA}$ , $V_{CC} = 3\text{V}$	4.2 2.3			V V
$I_{IL}$	Input Leakage Current I/O Pin	$V_{CC} = 5.5\text{V}$ , pin low (absolute value)			1	$\mu\text{A}$
$I_{IH}$	Input Leakage Current I/O Pin	$V_{CC} = 5.5\text{V}$ , pin high (absolute value)			1	$\mu\text{A}$
$R_{RST}$	Reset Pull-up Resistor		30		60	$\text{k}\Omega$
$R_{pu}$	I/O Pin Pull-up Resistor		20		50	$\text{k}\Omega$
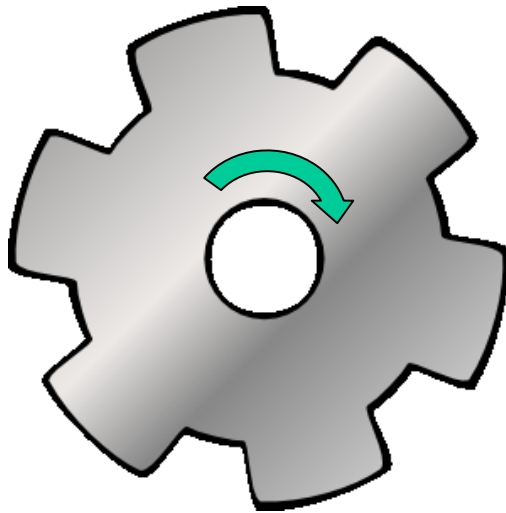
# Ex: Sensor (transmitter) with *open collector output*

Inductive proximity sensor  
(for ferrous metals)



Magnetic field

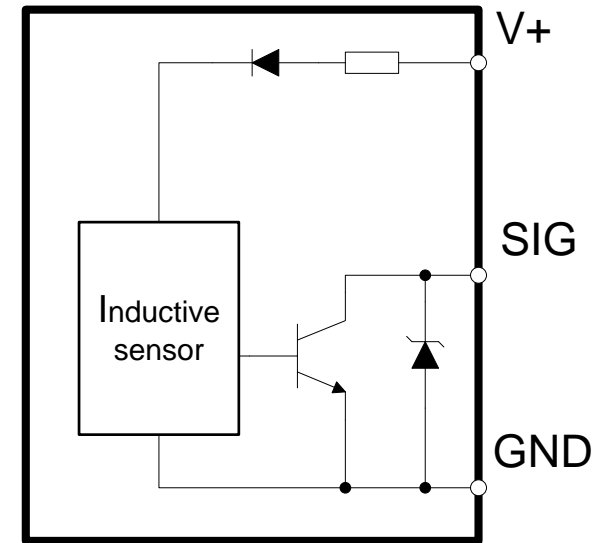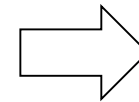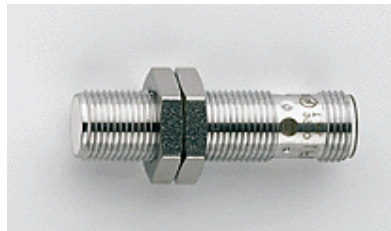


# How to drive a LED from an MCU


- example from an exam...

## Problem 1. (30 %)

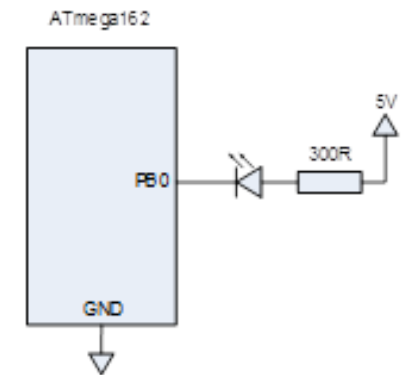
- a. Figure 1 shows the diagram of the 16 bit Timer/Counter unit of the Atmel AVR ATmega162 microcontroller. Assume that the system clock is driven by a 4.194304MHz external crystal oscillator and that Timer/Counter 1 is set to normal mode and clocked ( $\text{clk}_{T1}$ ) by the system clock prescaled by a value of 64. Calculate the frequency of the TOV1 interrupt  $f_{\text{TOV1}}$  (timer overflow).
- b. A blinking LED is frequently used to show the “heart beat” of an embedded computer indicating that the system runs normally. Show with a simple circuit diagram how a heart beat LED can be connected to pin PB0 of the Atmel AVR ATmega162 enabling the microcontroller to alternately sink a 10mA current through the LED. The supply voltage of the microcontroller is 5V and the forward voltage drop of the LED is 2V. See Figure 4 for the pinout of the ATmega162.
- c. Use the TOV1 interrupt from a) and write a simple program in C/pseudo-code that implements the heart beat LED from b) and a mechanism that keeps track of how many hours and days the system has been running since last reset.




# INDUSTRIAL EMBEDDED COMPUTER

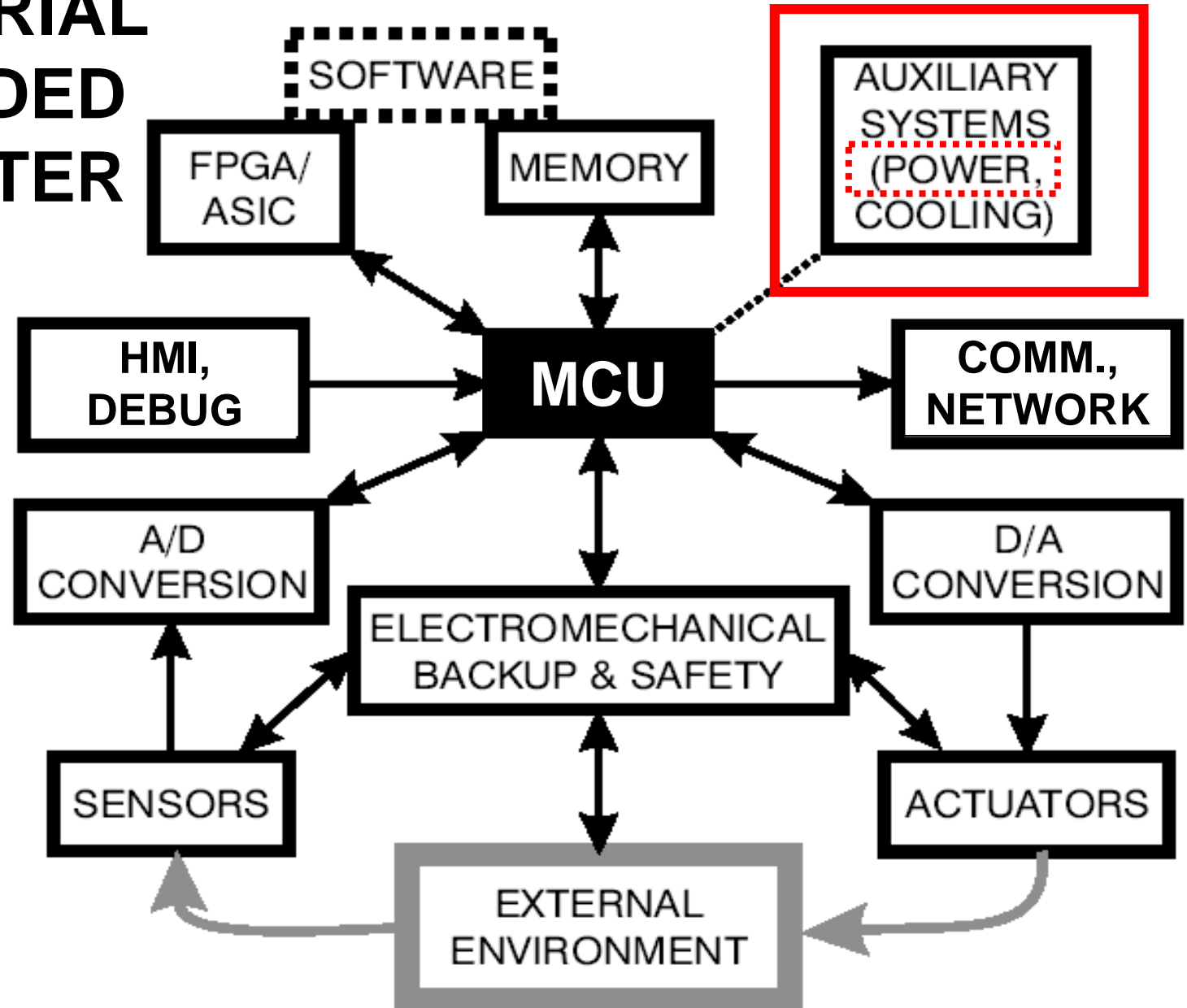

# Power supply

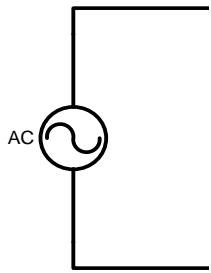


# Power supply

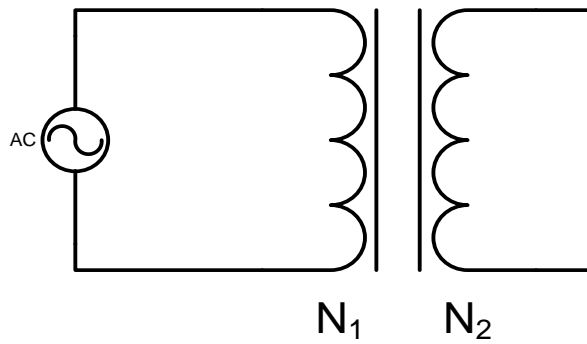





# Power supply

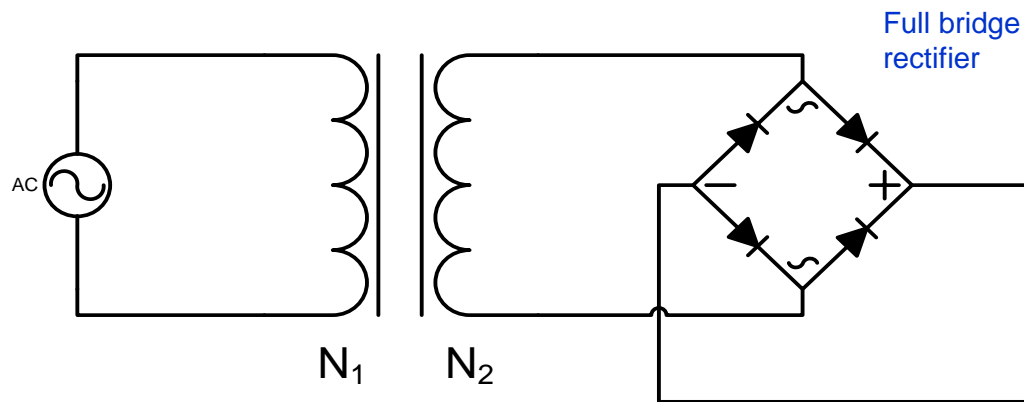


# Power supply

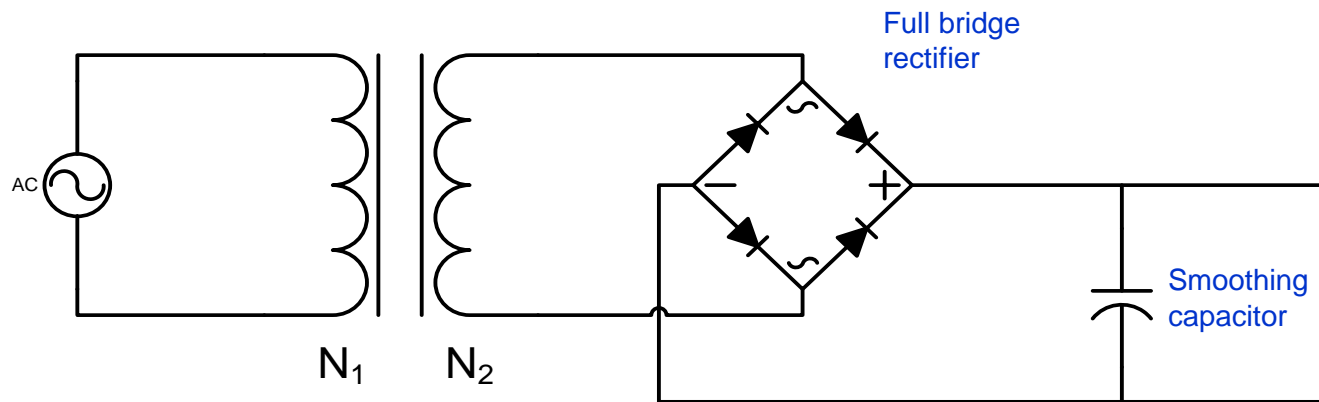


# Power supply

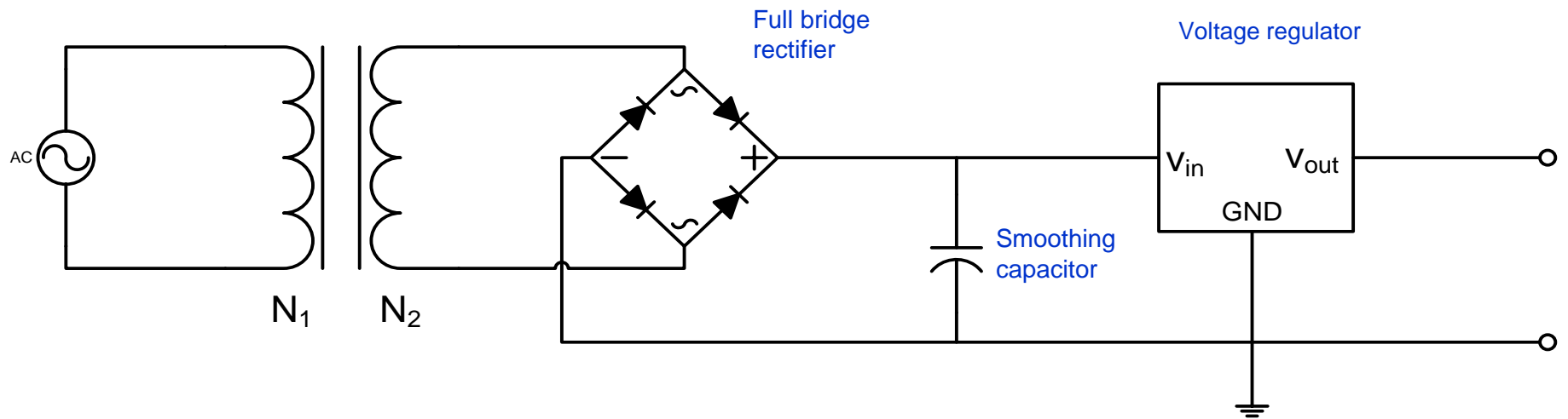

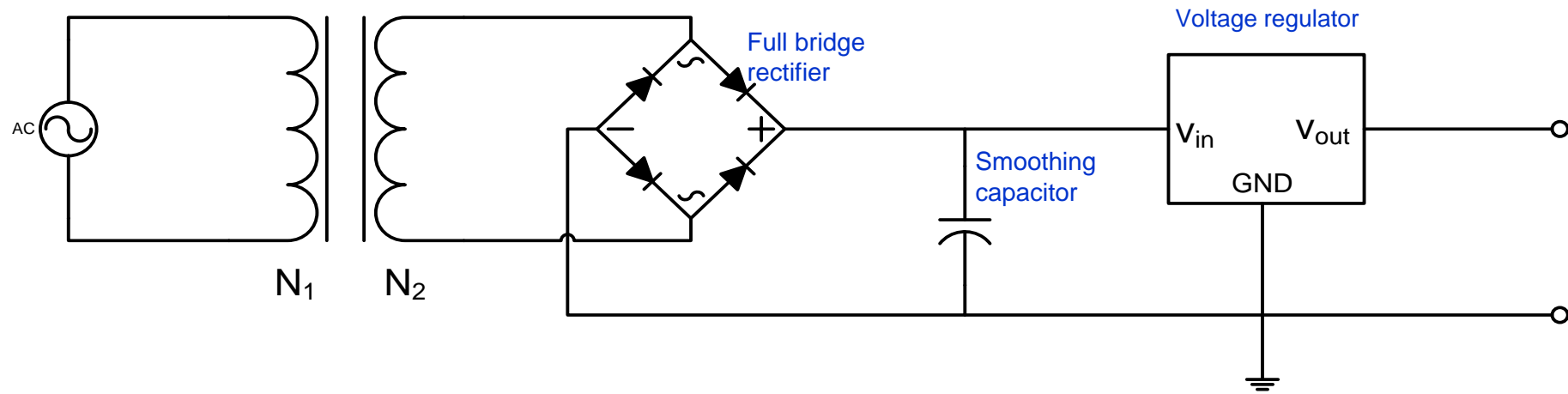

 
## Voltage regulator

- provides a *stable supply voltage*...
- at the *desired level*...
- and *sufficient power capacity*...
- independent of variations in input voltage and load current:
  - Line regulation ( =  $100 * \Delta V_{out} / \Delta V_{in}$  [%] )
  - Load regulation ( =  $100 * (V_{out-maxload} - V_{out-minload}) / V_{out-nomload}$  [%] )




## Linear regulator (principle)

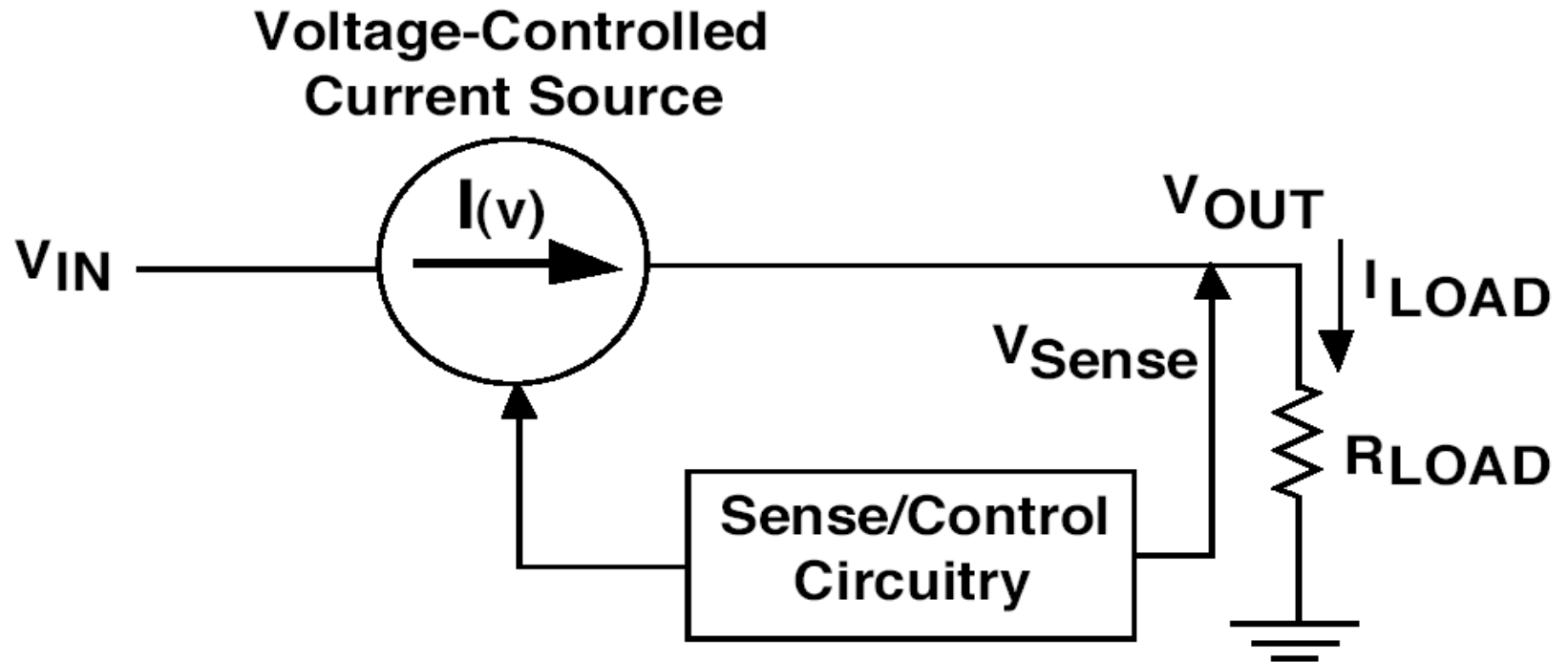


Three main types:

- Standard
- LDO (Low DropOut)
- Quasi LDO

# Linear regulator, standard type



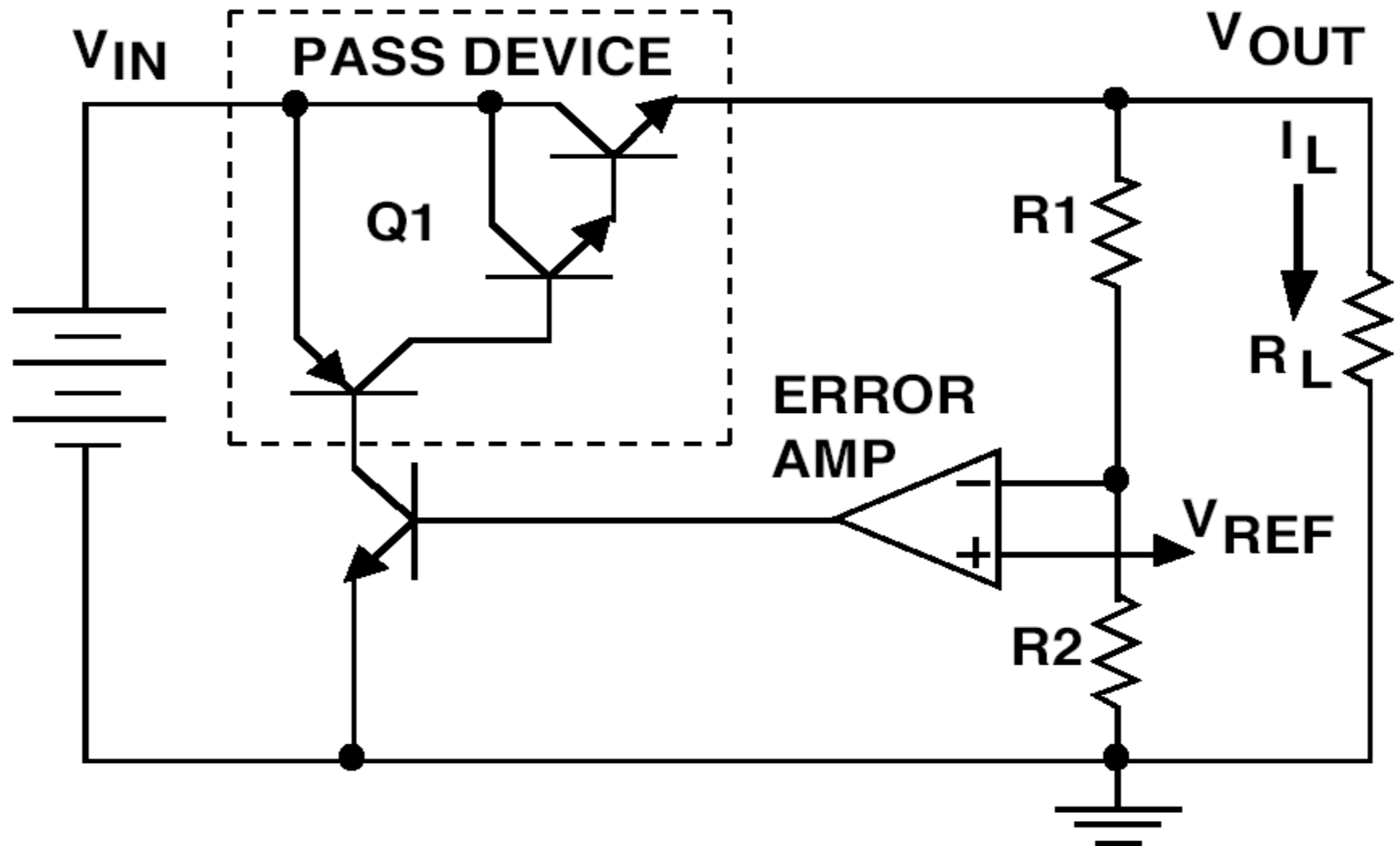


# LDO regulator


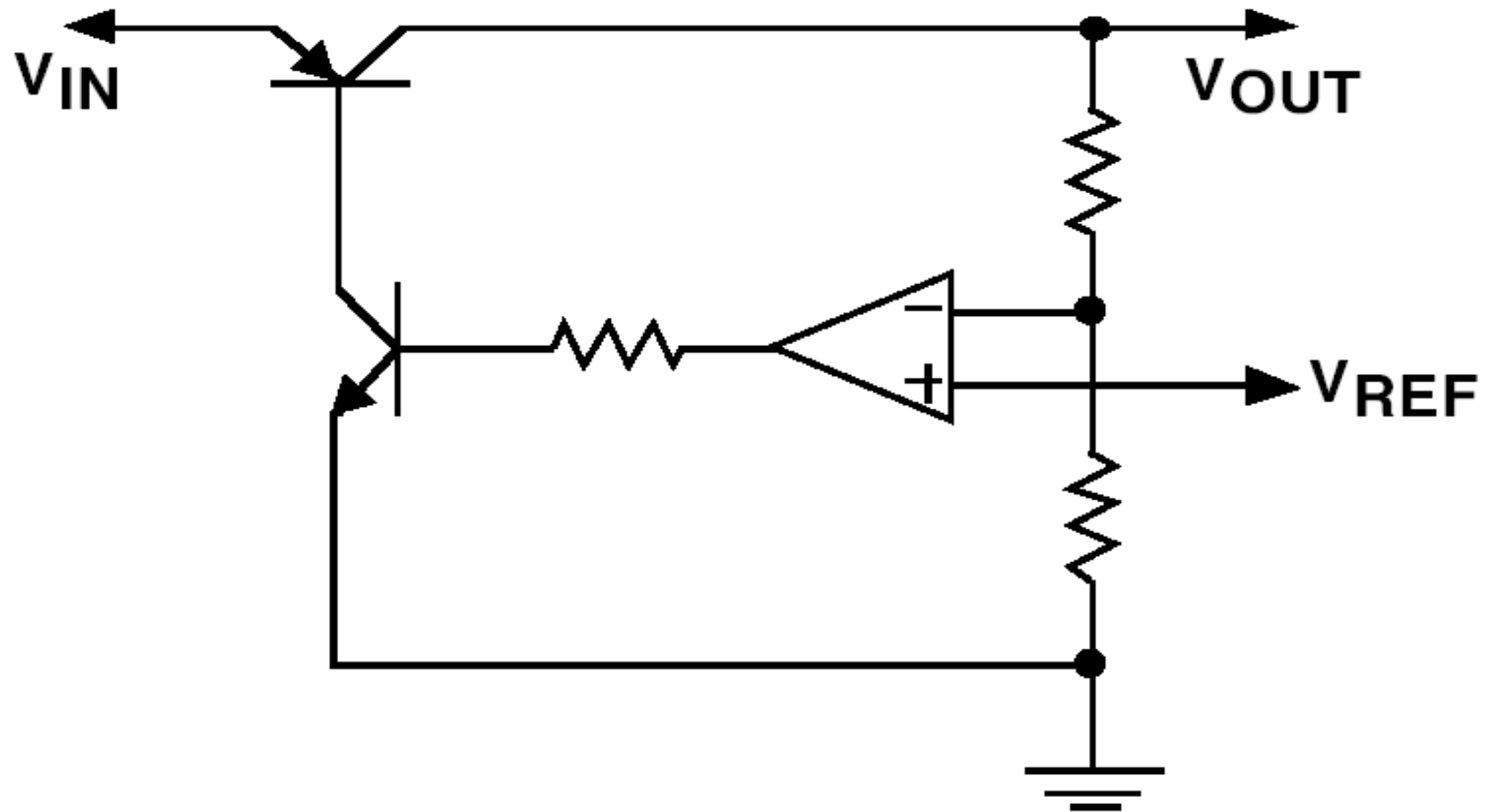




# Switching regulator (Buck)

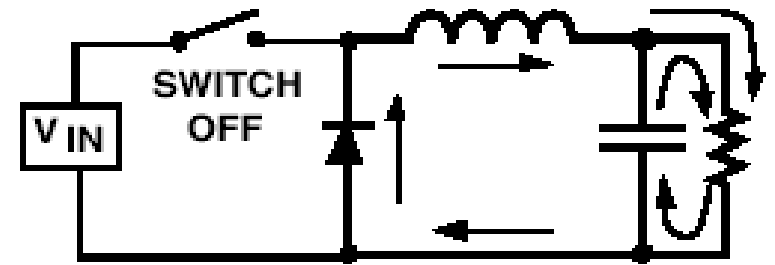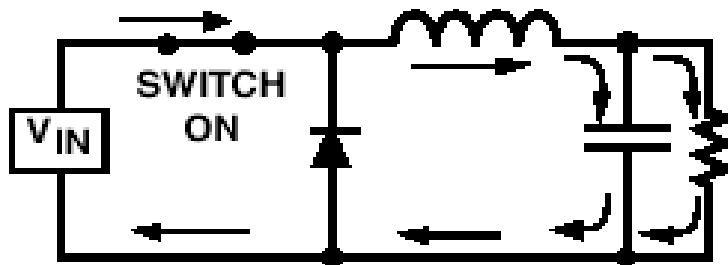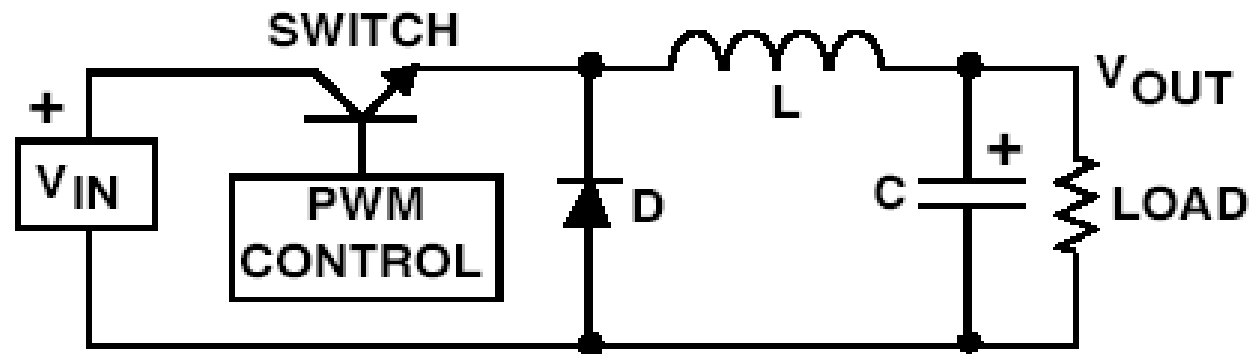


# Switching regulator (Buck)

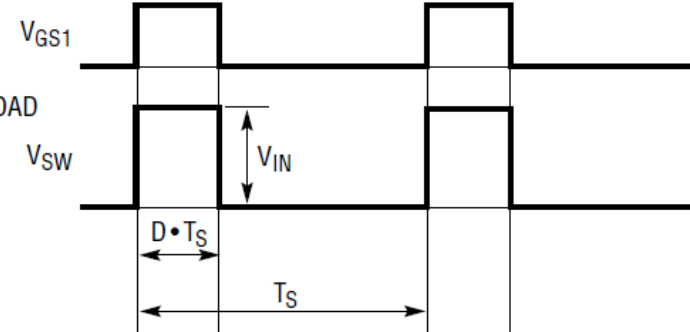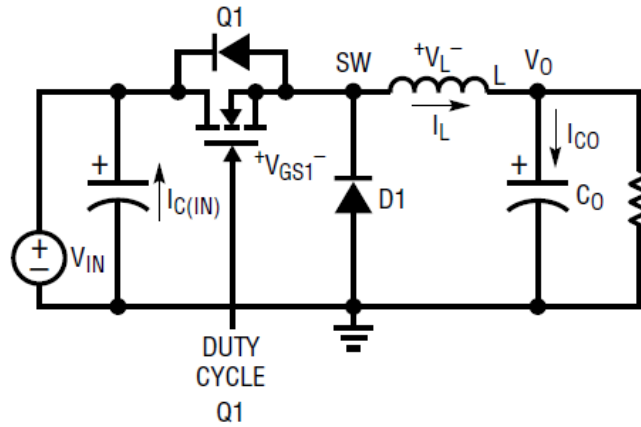


PWM:  
 $0 < D < 1$


# Switching regulator (Buck)

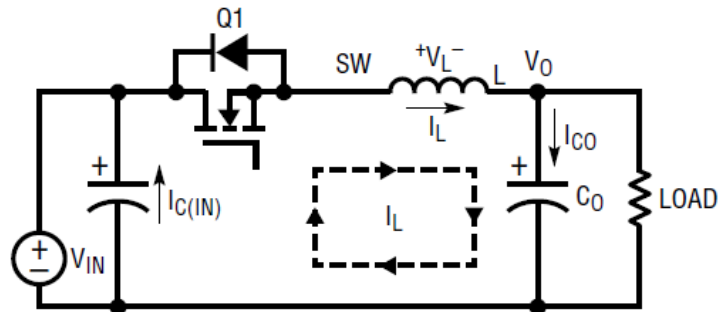


A. INDUCTOR CHARGING MODE

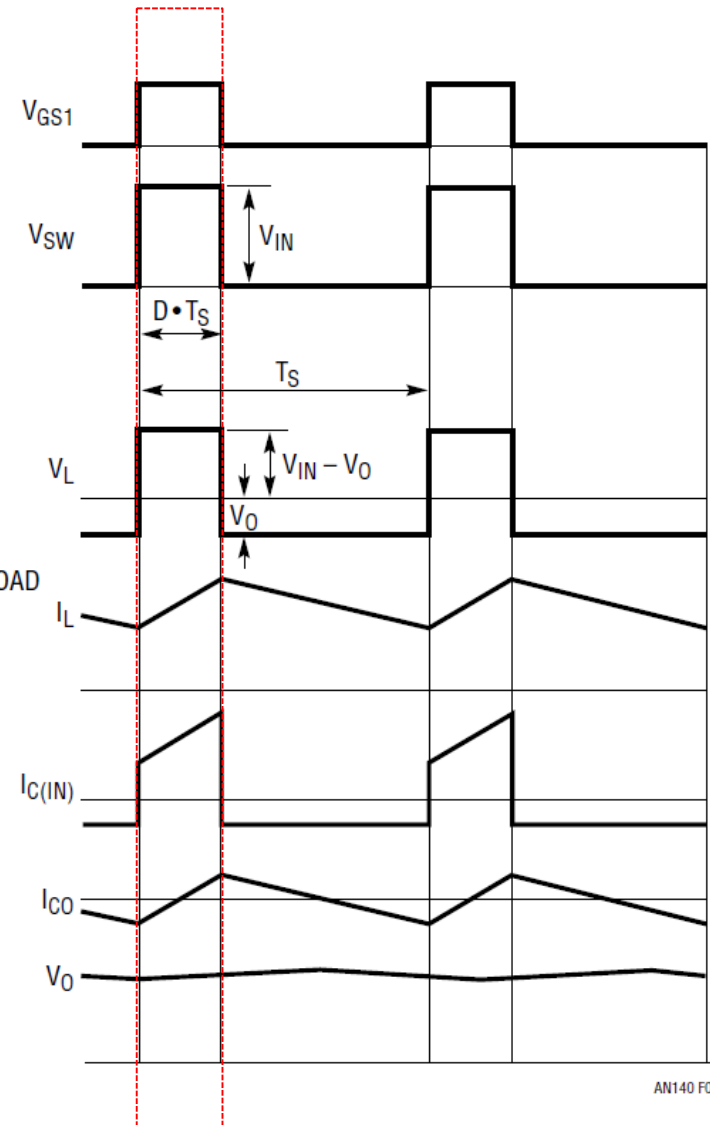

# Switching regulator (Buck)



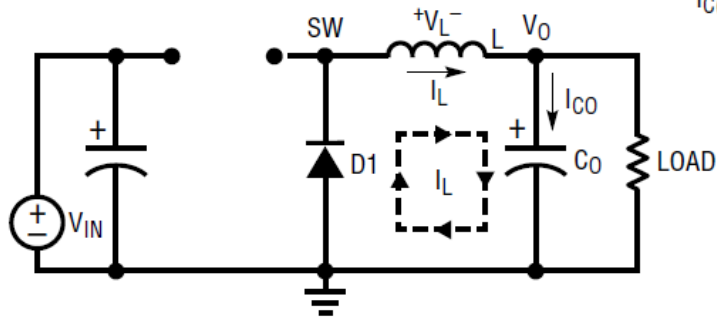


B. INDUCTOR DISCHARGING MODE

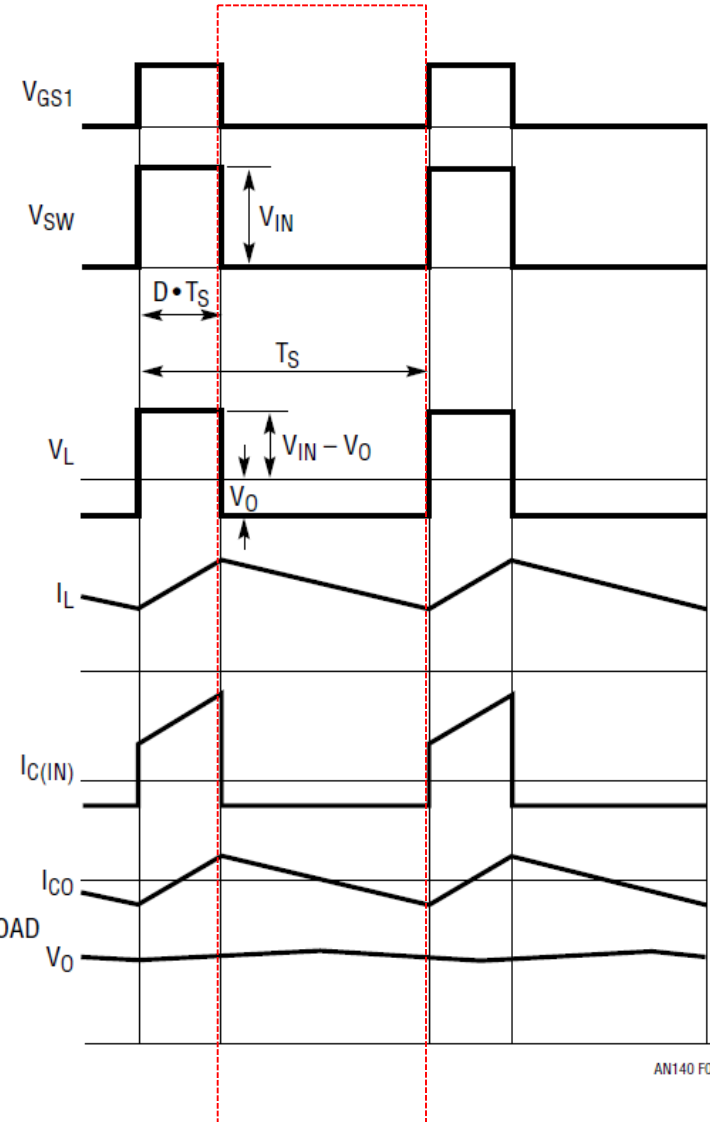

AN140 F08

## Switching regulator (Boost)

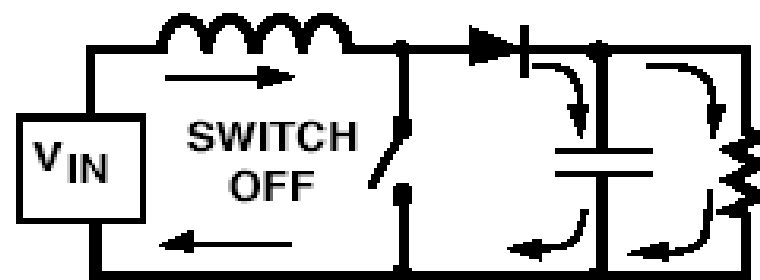
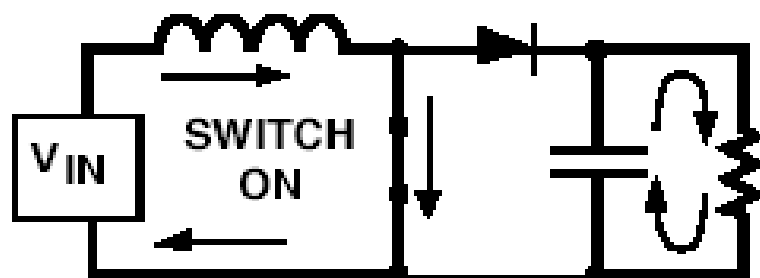
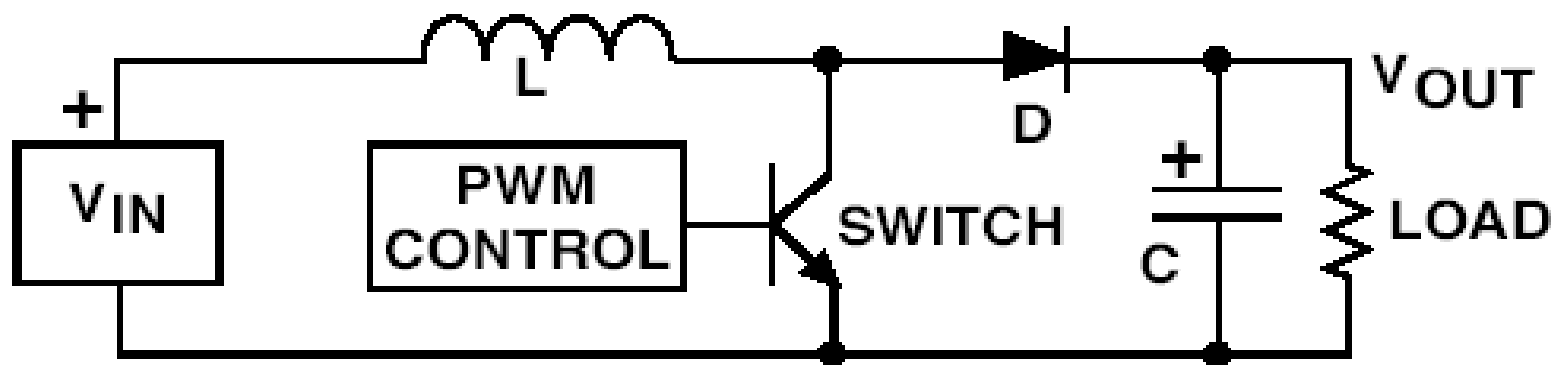


# Design considerations switching regs.


Remember that switching regulators are relatively noisy:

- Output ripple (10 - 100 mV typical,  $f_{\text{PWM}}$ )
- Supply ripple ( $f_{\text{PWM}}$ )
- Switching current in inductor causes radiation of el. noise

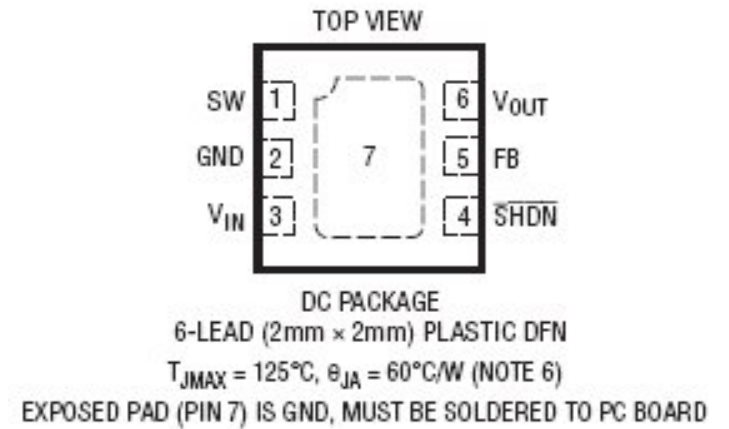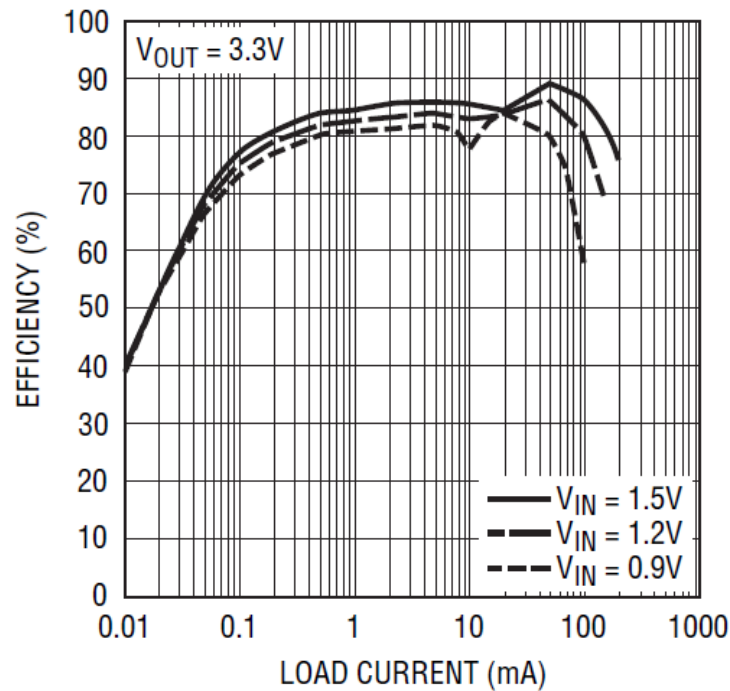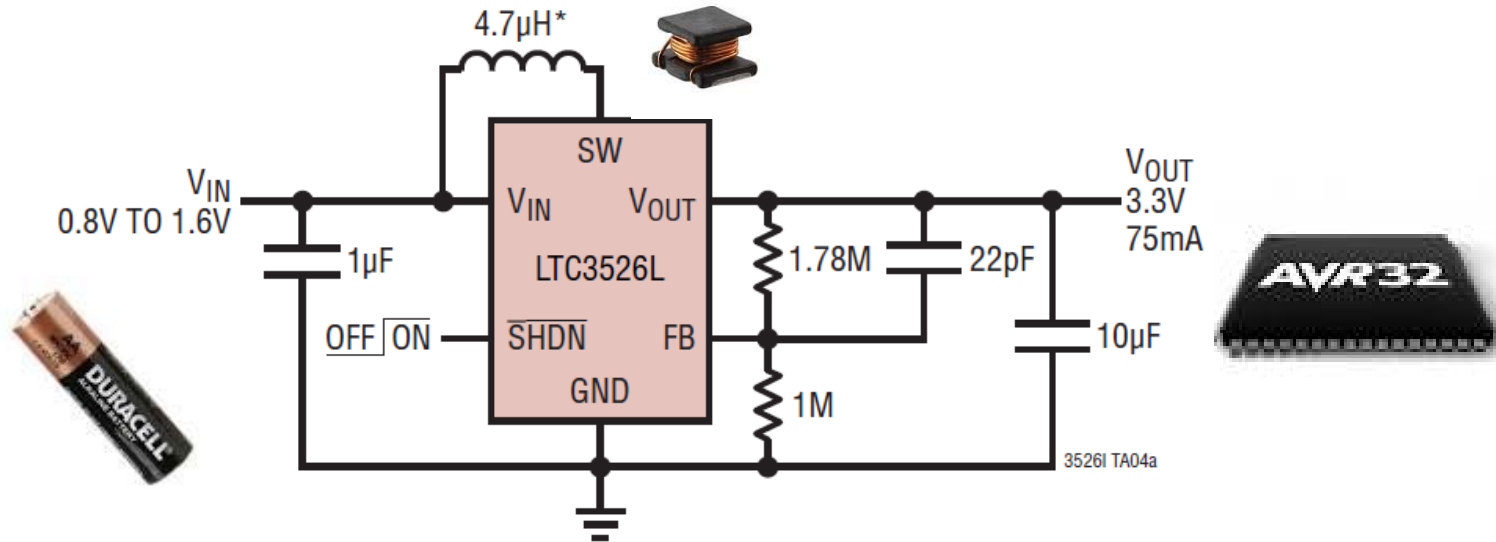Circuits operating with low level signals (<100  $\mu\text{V}$  typ.) must take special care to avoid problems!



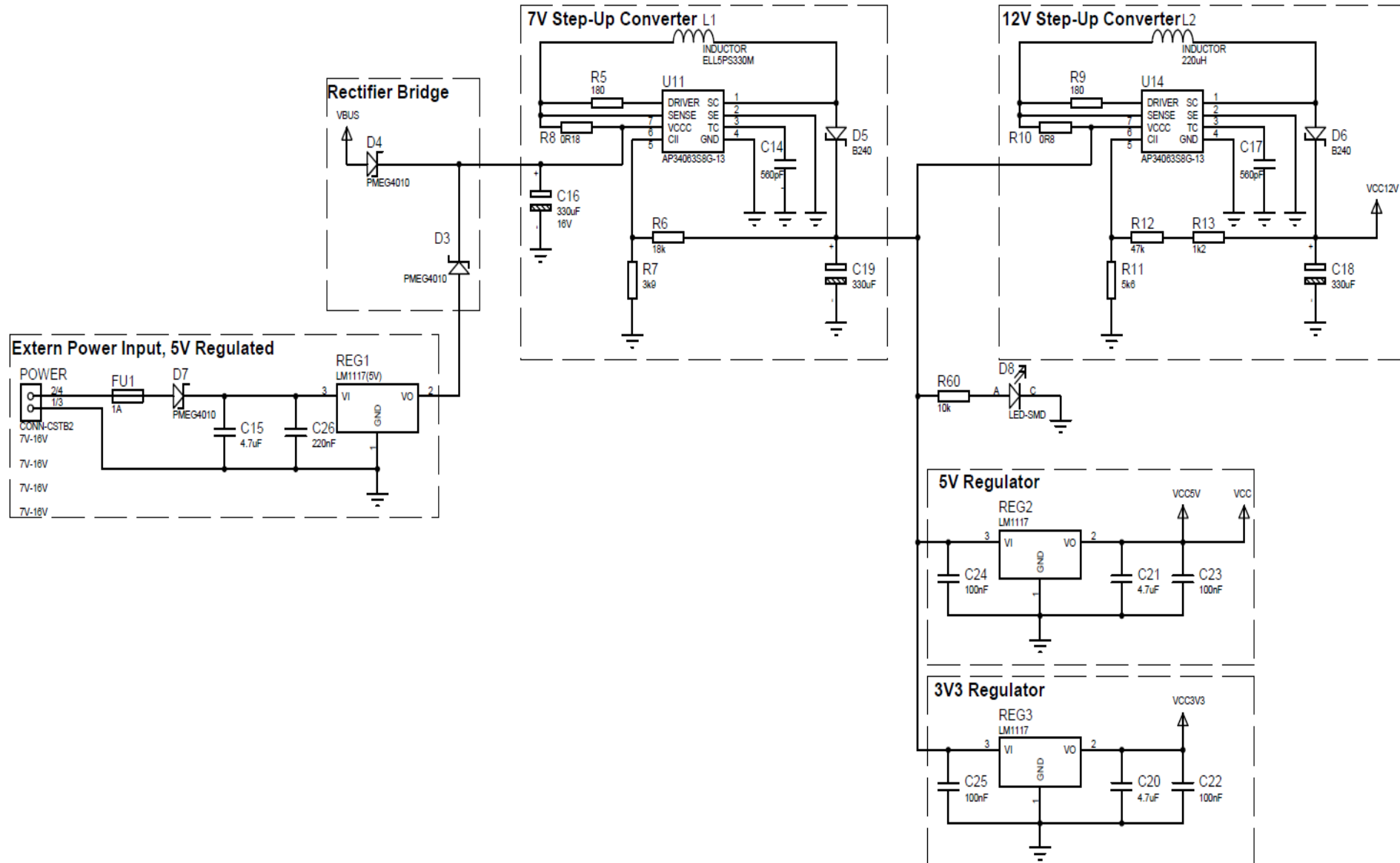
# Example: Voltage regulation on USB multifunction node





# Charge pump ("Flying capacitor")


- Inductorless DC/DC converters
  - Buck, boost, inverting
  - Low current

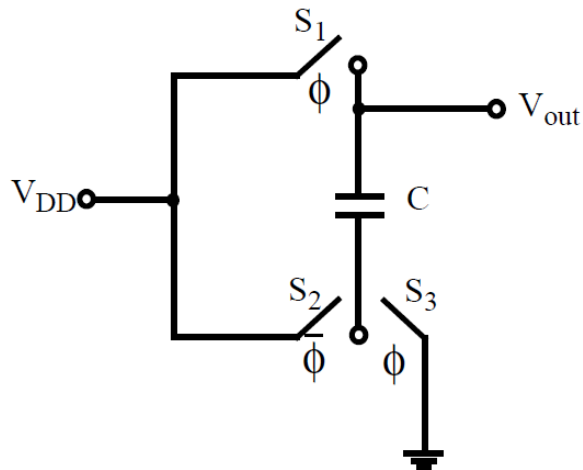

**Fig. 1.** Simple voltage doubler

$$(V_{out} - V_{DD}) \cdot C = V_{DD} \cdot C$$

$$V_{out} = 2 \cdot V_{DD}$$

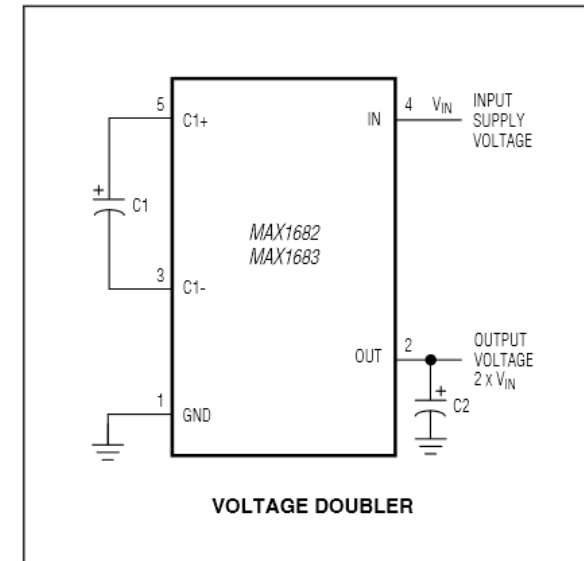

- $V_{in}$ : +2.0V to +5.5V
- $I_{out}$ : < 45mA
- Efficiency: 98%

# Example: RGB LED driver

## RGB Power Supply and Current Control

